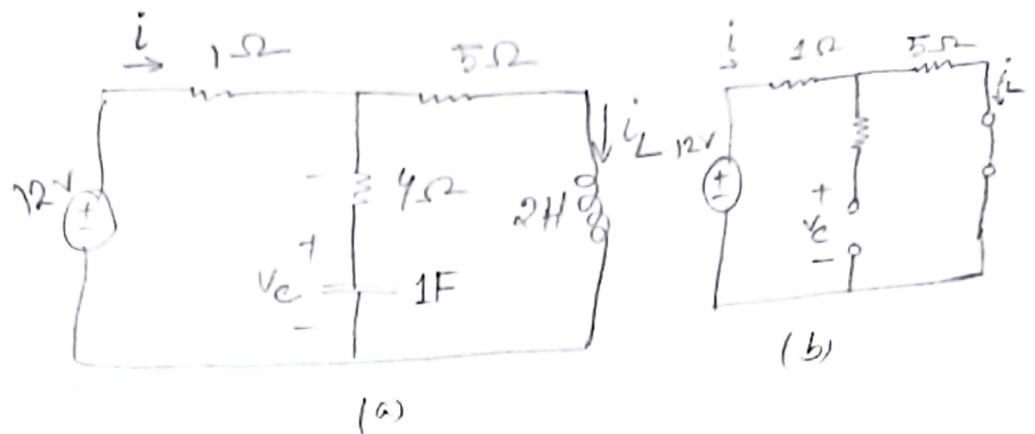


Example-6.10 :



Consider the circuit in Fig 6.27(a). Under dc conditions, find: (a) i , v_c and i_L (b) the energy stored in the capacitor and inductor.

Solution:

(a)

Here, $i = i_L$, $i = \frac{V}{R} = \frac{12V}{6\Omega} = 2A$

$R = (1 + 5)\Omega = 6\Omega$ $\therefore i_L = 2A$

The $\therefore$ voltage v_c is the same as the voltage across the 5Ω resistor. Hence,

$v_c = 5i = 5 \cdot 2 = 10V$

(b) The energy in the capacitor is,


$$\begin{aligned} W_c &= \frac{1}{2} C V_c^2 \\ &= \frac{1}{2} (1) (10)^2 \\ &= 50 \text{ J} \end{aligned}$$

The energy in the inductor is,


$$\begin{aligned} W_L &= \frac{1}{2} L i_L^2 \\ &= \frac{1}{2} (2) (2)^2 \\ &= 4 \text{ J} \end{aligned}$$

Practice Problem-6.10:

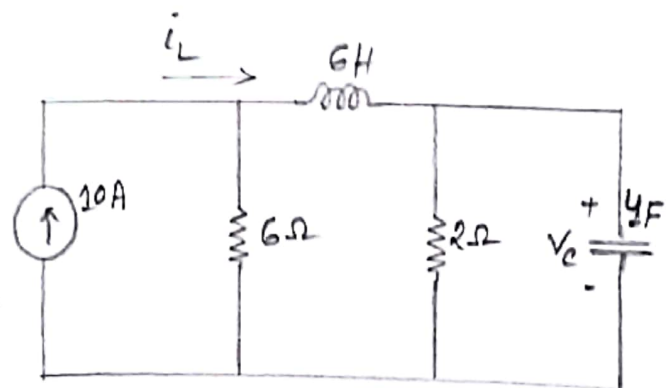Determine V_c , i_L and the energy stored in the capacitor and inductor in the circuit under dc conditions.



Solution:

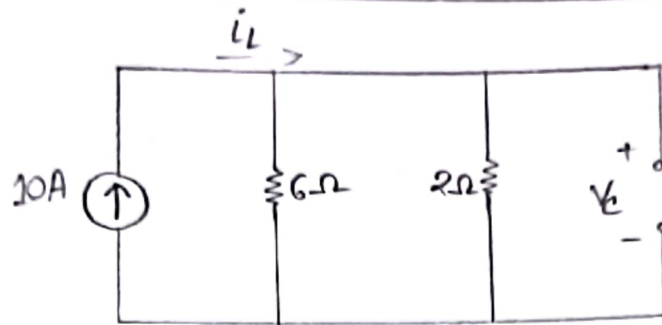

$$i_L = 10 \times \frac{6}{6+2} = \frac{60}{8} = 7.5A$$

$$V_C = 7.5 \times 2 = 15V$$

Energy of Capacitors:

$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} (4) (15)^2 = 450J$$

Energy of Inductors:

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (6) (7.5)^2 = 168.75J$$

Example - 9.1:

Find the amplitude, phase, period and frequency of the sinusoid.

$$v(t) = 12 \cos(50t + 10^\circ)$$

Solution:

Compare $v(t) = 12 \cos(50t + 10^\circ)$ with $v(t) = V_m \cos(\omega t + \phi)$
we get,

Amplitude, $V_m = 12 \text{ V}$

phase angle, $\phi = 10^\circ$

Angular frequency, $\omega = 50 \text{ rad/s}$

Time period, $T = \frac{2\pi}{\omega} = \frac{2\pi}{50} = 0.1257 \text{ s}$

Frequency, $f = \frac{1}{T} = \frac{1}{0.1257} = 7.958 \text{ Hz}$

Practice Problem-9.1:

Given the sinusoid $30 \sin(4\pi t - 75^\circ)$, calculate its amplitude, phase, angular frequency, period and frequency.

Solution:

$$V(t) = 30 \sin(4\pi t - 75^\circ)$$

Amplitude, $V_m = 30 \text{ V}$

Phase angle, $\phi = -75^\circ$

Angular frequency, $\omega = 4\pi = 12.57 \text{ rad/s}$

Time period, $T = \frac{2\pi}{\omega} = 0.5 \text{ s}$

frequency, $f = \frac{1}{T} = 2 \text{ Hz}$

Example - 9.2:

Calculate the phase angle between $v_1 = -10 \cos(\omega t + 50^\circ)$ and $v_2 = 12 \sin(\omega t - 10^\circ)$. state which sinusoid is leading.

Solution:

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

Convert V_1 into sin form,

$$V_1 = 10 \sin(\omega t + 50^\circ - 90^\circ)$$

$$= 10 \sin(\omega t - 40^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

From V_1 and V_2 ,

$$-10^\circ > -40^\circ$$

Hence the angle of V_2 is greater than the angle of V_1 .

$\therefore V_2$ leads V_1 by 30° .

Practice Problem - 9.2:

Find the phase angle between

$$i_1 = -4 \sin(377t + 55^\circ) \text{ and } i_2 = 5 \cos(377t - 65^\circ)$$

Does i_1 lead or lag i_2 ?

Solution:

Express i_1 in cosine form,

$$\begin{aligned} i_1 &= 4 \cos(377t + 55^\circ + 90^\circ) \\ &= 4 \cos(377t + 145^\circ) \end{aligned}$$

$$i_2 = 5 \cos(377t - 65^\circ)$$

From i_1 & i_2 , $145^\circ > -65^\circ$


Hence $i_1 > i_2$. $\therefore$ phase angle $= 145^\circ - (-65^\circ)$
 $= 210^\circ$

$\therefore i_1$ leads i_2 by $145^\circ - 210^\circ$.

Example - 9.9:

Find $v(t)$ and $i(t)$ in the circuit.

$$v_s = 10 \cos 4t$$

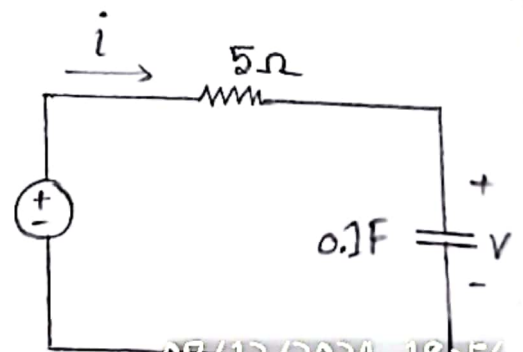

Solution:

$$V_s = 10 \angle 0^\circ$$

$$\omega = 4$$

$$\text{Impedance, } Z = 5 + \frac{1}{j\omega C}$$

$$= 5 + \frac{1}{j 4 \times 0.1}$$

$$= 5 - j2.5 \Omega$$

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5 - j2.5} = \frac{10 \angle 0^\circ}{5.59 \angle -26.56^\circ}$$

$$= 1.789 \angle 26.56^\circ A$$

$$V = I Z_c = I \times \frac{1}{j\omega C} = \frac{1.789 \angle 26.56^\circ}{j 4 \times 0.1}$$

$$= \frac{1.789 \angle 26.56^\circ}{0.4 \angle 90^\circ}$$

$$= 4.46 \angle -63.43^\circ V$$


$$\therefore V(t) = 4.46 \cos(4t - 63.43^\circ) V$$

$$I(t) = 1.789 \cos(4t + 26.56^\circ) A$$



Practice Problem: 9.9:

Determine $v(t)$ and $i(t)$.

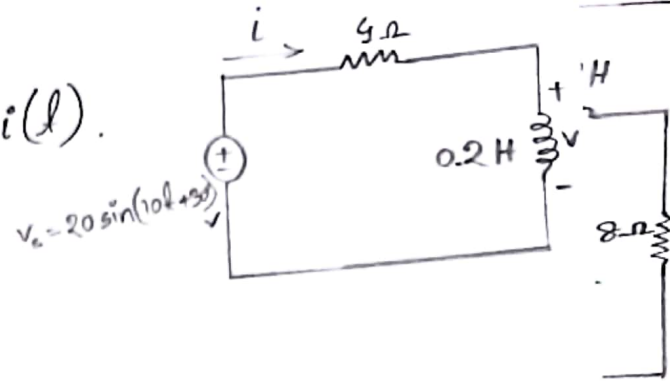

Solution:

$$V_s = 20 \angle 30^\circ$$

$$\omega = 10$$

$$Z = 4 + j\omega L = 4 + (j10 \times 0.2)$$

$$= 4 + j2$$

$$= 4.47 \angle 26.56^\circ$$

$$I = \frac{V_s}{Z} = \frac{20 \angle 30^\circ}{4.47 \angle 26.56^\circ} = 4.47 \angle 3.44^\circ$$

$$V = I Z_L = (4.47 \angle 3.44^\circ) \times j\omega L$$

$$= (4.47 \angle 3.44^\circ) \times j10 \times 0.2$$


$$= 8.94 \angle 93.44^\circ$$

$$\therefore v(t) = 8.94 \sin(10t + 93.44^\circ) \text{ V}$$

$$i(t) = 4.47 \sin(10t + 3.44^\circ) \text{ A}$$

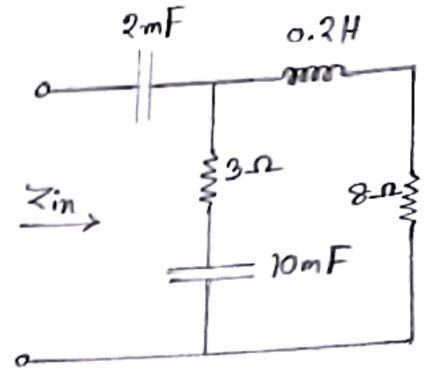Example - 9.10:

Find the input impedance of the circuit. Assume that the circuit operates at $\omega = 50 \text{ rad/s}$.



Solution: $\omega = 50 \text{ rad/s}$

$$Z_{C_1} = \frac{1}{j\omega C_1} = \frac{1}{j50 \times 2 \times 10^{-3}} = -10j \Omega$$

$$Z_{C_2} = \frac{1}{j\omega C_2} = \frac{1}{j50 \times 10 \times 10^{-3}} = -2j \Omega$$

$$Z_L = j\omega L = j50 \times 0.2 = j10 \Omega$$

Now,

$$Z_1 = Z_L + 8\Omega = j10 + (8 + j10)\Omega$$


$$Z_2 = 3\Omega + Z_{C_2} = (3 - j2)\Omega$$

$$\begin{aligned} Z_3 = Z_1 \parallel Z_2 &= \frac{(8 + j10)(3 - j2)}{8 + j10 + 3 - j2} \\ &= \frac{(8 + j10)(3 - j2)}{11 + 8j} \\ &= \frac{44 + 14j}{11 + 8j} \end{aligned}$$

$$\begin{aligned}
 Z_{in} &= Z_{C1} + Z_2 = -j10 + \frac{44 + 14j}{11 + 8j} \\
 &= (3.22 - j11.07) \Omega
 \end{aligned}$$

Practice Problem - 9.10:

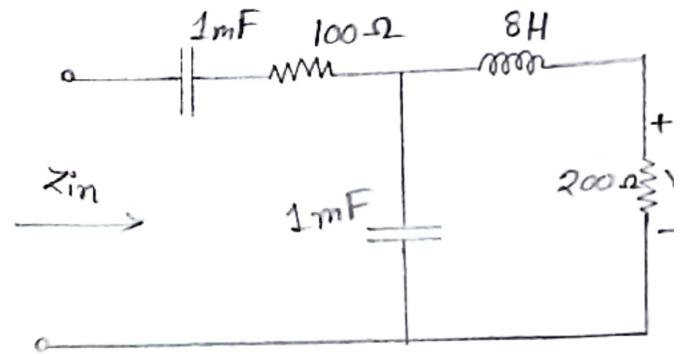Determine the input impedance of the circuit at $\omega = 10 \text{ rad/s}$.



Solution: $\omega = 10 \text{ rad/s}$

$$Z_{C_{1mF}} = \frac{1}{j\omega C} = \frac{1}{j10 \times 1 \times 10^{-3}} =$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j10 \times 1 \times 10^{-3}} = -100j$$

$$Z_1 = 100 + \frac{1}{j10 \times 1 \times 10^{-3}} = 100 - 100j$$

$$Z_2 = 200 + (j10 \times 8) = 200 + 80j$$